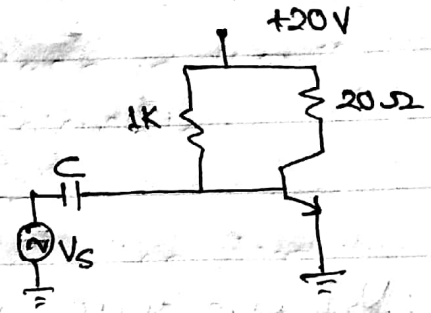


Calculate Power loss in transistor, collector efficiency, overall efficiency of given ckt. Assume $\beta = 25$ & base current at peak is 10 mA .

Soln: Given,

$$V_{CC} = 20 \text{ V}, R_C = 20 \Omega, R_B = 1 \text{ K}, \beta = 25$$

$$I_{BP} = 10 \text{ mA}$$



Applying KVI at I/p,

$$V_{CC} = I_B R_B + V_{BE}$$

$$\Rightarrow I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{(20 - 0.7) \text{ V}}{1 \text{ K}} = 19.3 \text{ mA}$$

And we know, $I_C = \beta I_B$

$$\text{So, } I_{CQ} = \beta I_{BQ} = 25 \times 19.3 = 0.48 \text{ A}$$

$$\text{I/p Power (} P_{in(dc)} \text{)} = V_{CC} I_{CQ} = 20 \text{ V} \times 0.48 \text{ A} = 9.6 \text{ W}$$

$$\text{O/p Power, } P_o(ac) = V_{CE,rms} \times I_{C,rms}$$

$$= \frac{V_{CE,P} \times I_{CP}}{2}$$

$$= \frac{I_{CP} R_C \times I_{CP}}{2} = \frac{I_{CP}^2 R_C}{2}$$

$$= \frac{(0.25)^2 \times 20}{2} = 0.625 \text{ W}$$

$$\text{where, } I_{CP} = \beta I_{BP} = 25 \times 10 \text{ mA} = 0.25 \text{ A}$$

$$\therefore \text{Power Loss in transistor} = V_{CC} I_{CQ} - I_{CQ}^2 R_C$$

$$= 20 \times 0.48 - (0.48)^2 \times 20$$

$$= 4.99 \text{ W}$$

= avg DC power dissipated at collector.

$$\text{ii) Collector Efficiency } (\eta_c) = \frac{\text{avg ac power delivered to load}}{\text{avg dc power dissipated at collector}} \times 100\%$$

$$= \frac{0.625}{4.99} \times 100\%$$

$$= 12.52\%$$

$$\text{iii) Overall Efficiency } (\eta) = \frac{P_o(\text{ac})}{P_{in}(\text{dc})} \times 100\%$$

$$= \frac{0.625}{9.6} \times 100\%$$

$$= 6.51\%$$

For a class B amp providing a 20V peak signal to the 16Ω load and a power supply of $V_{cc} = 30\text{V}$. Find I_p and o/p power and efficiency also.

Soln:

Given, $V_{LP} = 20\text{V}$

$R_L = 16\Omega$

$V_{cc} = 30\text{V}$

i) I_p power, $P_{in}(\text{dc}) = \frac{V_{cc} \times I_{dc}}{1}$

$$= V_{cc} \times \frac{I_{CP}}{\pi} = V_{cc} \frac{V_{LP}}{R_L \pi}$$

$$= 30 \times \frac{20}{16 \times \pi} = 11.94\text{W}$$

ii) O/p Power, $P_o(\text{ac}) = \frac{1}{4} I_{CP} V_{cc}$


$$= \frac{1}{4} \times \frac{V_{LP}}{R_L} \times V_{cc}$$

$$= \frac{1}{4} \times \frac{20}{16} \times 30 = 9.375\text{W}$$

iii) Efficiency, $\eta = \frac{P_o(\text{ac})}{P_{in}(\text{dc})} \times 100\% = \frac{9.375}{11.94} \times 100\% = 78.5\%$

A class A amp biased at $V_{CE} = 12V$ is as shown in fig below. The op voltage is maxm possible without distortion. Calculate,

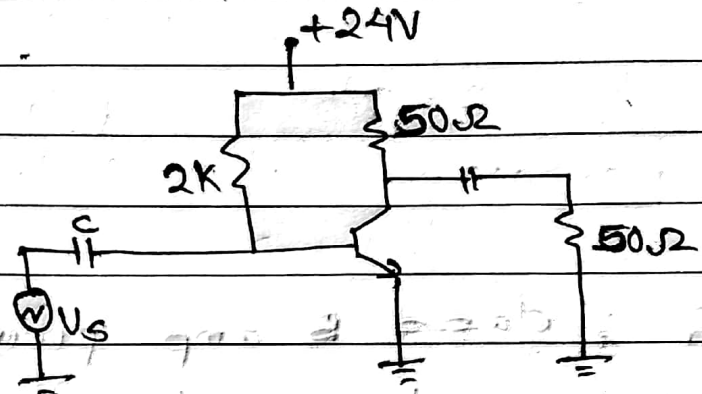- i) average dc power from source
- ii) average ac power delivered to the load.
- iii) collector efficiency.
- iv) overall efficiency.



Sol: Given,

$$V_{CC} = 24V, V_{CEQ} = 12V, R_B = 2k, R_C = R_L = 50\Omega$$

We have,

$$V_{CC} = I_{CQ} R_C + V_{CEQ}$$

$$\Rightarrow I_{CQ} = \frac{V_{CC} - V_{CEQ}}{R_C} = \frac{24 - 12}{50} = 0.24 A$$

i) Avg dc I_P power from Source,

$$P_{in(dc)} = V_{CC} \times I_{CQ}$$

$$= 24 \times 0.24$$

$$= 5.76 W$$

ii). Avg ac power delivered to load

$$P_{o(ac)} = V_{CE,rms} \times I_{C,rms}$$

$$= \frac{V_{CEP} I_{CP}}{2}$$


$$= \frac{(V_{CEP})^2}{2 R_C} = \frac{(V_{OP})^2}{2 R_C}$$

Here, $r_L = R_C // R_L$
 $= 50 // 50$
 $= \frac{50 \times 50}{50 + 50}$
 $= 25 \Omega$

Thus, $V_{op} = I_{CQ} \times r_L$
 $= 0.24 \times 25$
 $= 6V$

So,

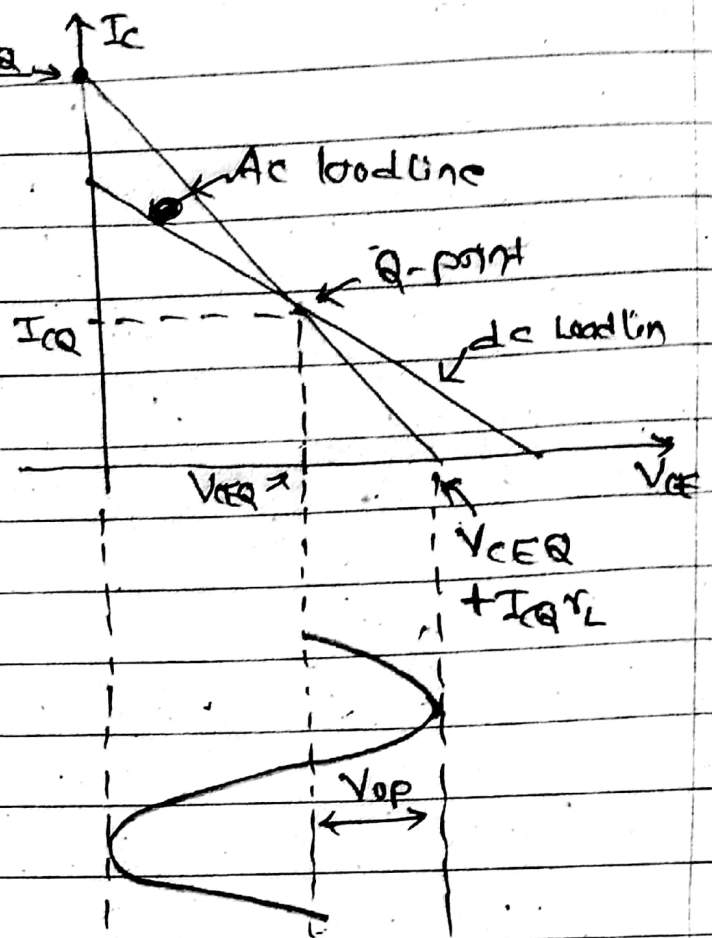$P_o(ac) = \frac{(V_{op})^2}{2R_C}$
 $= \frac{6^2}{2 \times 50}$
 $= 0.36W$



ii) Overall Efficiency, $\eta = \frac{P_o(ac)}{P_{in}(dc)} \times 100\%$
 $= \frac{0.36}{5.76} \times 100\%$
 $= 6.25\%$

iii) Collector efficiency,

$\eta_c = \frac{\text{avg ac power delivered to load}}{\text{avg dc power dissipated at collector}} \times 100\%$

where,

avg dc power dissipated at collector $= V_{CEQ} \times I_{CQ}$
 $= 12V \times 0.24A$
 $= 2.88W$

$\therefore \eta_c = \frac{0.36}{2.88} = 12.5\%$


2018 Fall

$$V_{CC} = 12V$$

$$\Delta I_C = 100 \text{ mA}, \quad \Delta V_{CE(\text{max})} = 12V$$

$$R_L = 5\Omega$$
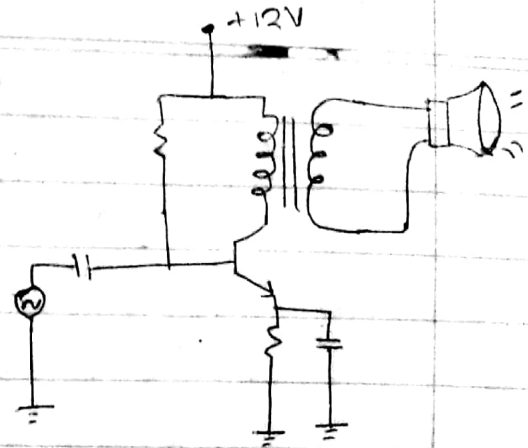
$$\text{Resistance of transistor} = \frac{\Delta V_{CE}}{\Delta I_C} = \frac{12V}{100 \text{ mA}} = 120\Omega$$



Let $n:1$ be the turn ratio of transformer.

& let R_L' be primary load resistance,

$$I_1^2 R_L' = I_2^2 R_L$$

$$\Rightarrow R_L' = \left(\frac{I_2}{I_1} \right)^2 R_L = \left(\frac{N_1}{N_2} \right)^2 R_L \quad \left[\because \frac{N_1}{N_2} = \frac{I_2}{I_1} = \frac{V_1}{V_2} \right]$$

$$\text{or, } R_L' = n^2 R_L$$

$$\text{or, } 120 = n^2 \times 5 \Rightarrow n^2 = 120/5$$

$$\Rightarrow n = 4.9$$

So, turn ratio = 4.9:1

Also, $\frac{N_1}{N_2} = \frac{V_1}{V_2}$ where, V_1 = Primary (i/p) voltage,
 V_2 = secondary voltage

$$\Rightarrow V_2 = \left(\frac{N_2}{N_1} \right) \times V_1 = \left(\frac{V_1}{N_1/N_2} \right) = \frac{V_1}{n}$$

$$= \frac{12}{4.9} = 2.47V$$

$$\& \text{ load current, } I_L = \frac{V_2}{R_L} = \frac{2.47V}{5\Omega} = 0.49A$$

$$\begin{aligned} \therefore \text{Power transferred to load} &= I_L^2 R_L \\ &= (0.49)^2 \times 5 \\ &= 1.2W \end{aligned}$$